

①

A

Quiz-2

Answer to the question no 1

1(a)

Basic components of module:

Basic components of modules are module name, Port list, Port declarations, reg, Variables, Data flow, Parameters. ~~Declaration~~ Declaration of wires, Instantiation of lower level modules, block, task and functions.

Mandatory components:

~~module~~ Mandatory components are module, module name, end module.

1 (b)

(2)

Depending on direction port modules are input, output, inout.

∴ The process of connecting the port is called the port connection technique.

(1) connection by order list

(2) connecting ports by name

Port connection rules

Module ~~can~~ communicate with external world with ports. There are some techniques for declaring the ports and some rules. They are given below.

③

① Inputs : Always it will be wire.
Externally they can be connected to variable.

② Outputs Output can be of reg or net type.
Externally they must be connected to a ~~net~~
net type variable.

③ Bidirectional ports : Always of type net
Externally, they must be ~~can~~ connected to
net type variable.

S	X	L	0	
X	X	0	1	0
X	X	1	0	1
X	X	X	X	0
X	X	X	X	1

Answer to the questions no 2

(4)

2 (a)

NAND

	0	1	x	z
0	1	1	1	1
1	1	0	x	x
x	1	x	x	x
z	1	x	x	x

XNOR

	0	1	x	z
0	1	0	x	x
1	0	1	x	x
x	x	x	x	x
z	x	x	x	x

(b)

(5)

module Subtractor (D, B, a, b, c)

Output D, B ;

input a, b, c ;

wire w1, w2, w3, w4

XOR #(t1:t4:t7) x1(a, b, c) ;

And

~~a1~~

not

n1(a) ;

a and #(t1:t4:t7) a1(b, w1) ;

a and #(t1:t4:t7) a2(c, w1) ;

a and #(t1:t4:t7) a3(b, c) ;

OR #(t1:t4:t7) o1(w2, w3, w4)